
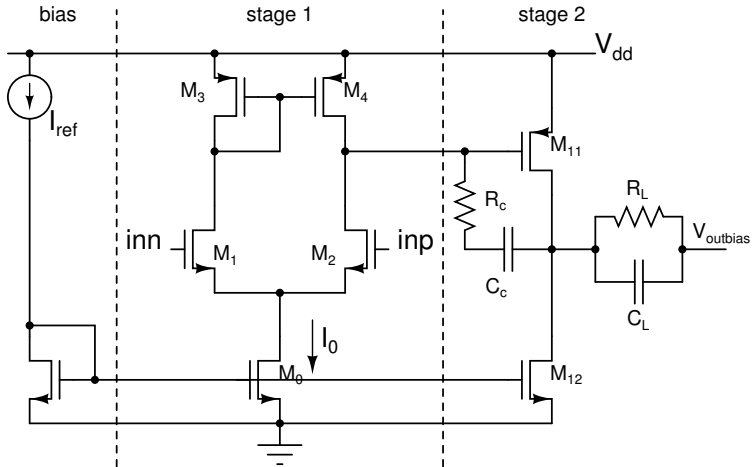


Two stage opamp

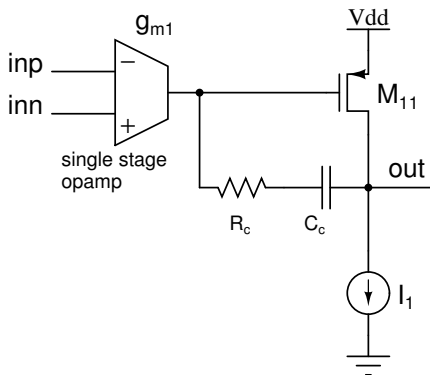

Two stage opamp



- First stage can be Differential pair, Telescopic cascode, or Folded cascode; Ideal g_{m1} assumed in the analysis
- Second stage: Common source amplifier
- Frequency response is the product of frequency responses of the first stage g_m and a common source amplifier driven from a current source

Common source amplifier: Frequency response

$$\frac{V_o(s)}{V_d(s)} = \left(\frac{g_{m1} g_{m11}}{G_1 G_L} \right) \frac{s C_c (R_c - 1/g_{m11}) + 1}{a_3 s^3 + a_2 s^2 + a_1 s + 1}$$

$$a_3 = \frac{R_c C_1 C_L C_c}{G_1 G_L}$$

$$a_2 = \frac{C_1 C_c + C_c C_L + C_L C_1 + R_c C_c (G_1 C_L + C_1 G_L)}{G_1 G_L}$$

$$a_1 = \frac{C_c (g_{m11} + G_1 + G_L + G_1 G_L R_c) + C_1 G_L + G_1 C_L}{G_1 G_L}$$

- G_1 : Total conductive load at the input
- G_L : Total conductive load at the output
- C_1 : Total capacitive load at the input
- C_L : Total capacitive load at the output

Common source amplifier: Poles and zeros

$$\begin{aligned}p_1 &\approx -\frac{G_1}{C_c\left(\frac{g_{m11}}{G_L} + 1 + \frac{G_1}{G_L} + G_1 R_c\right) + C_1\left(1 + \frac{G_1}{G_L}\right)} \\p_2 &\approx -\frac{g_{m11}\frac{C_c}{C_1+C_c} + G_L + G_1\frac{C_c+C_L}{C_1+C_c} + G_1 G_L R_c\frac{C_c}{C_1+C_c}}{\frac{C_1 C_c}{C_1+C_c} + C_L + \frac{R_c C_c (G_1 C_L + G_L C_1)}{C_c+C_L}} \\p_3 &\approx -\left(\frac{1}{R_c}\left(\frac{1}{C_L} + \frac{1}{C_c} + \frac{1}{C_1}\right) + \frac{G_1}{C_1} + \frac{G_L}{C_L}\right) \\z_1 &= \frac{1}{(1/g_{m11} - R_c)C_c}\end{aligned}$$

Unity gain frequency

$$\omega_u \approx \frac{g_{m1}}{C_c\left(1 + \frac{G_L}{g_{m11}} + \frac{G_1}{g_{m11}} + \frac{G_1 G_L R_c}{g_{m11}}\right) + C_1\left(\frac{G_L}{g_{m11}} + \frac{G_1}{g_{m11}}\right)}$$

Common source amplifier: Frequency response

- Pole splitting using compensation capacitor C_c
 - p_1 moves to a lower frequency
 - p_2 moves to a higher frequency (For large C_c , $p_2 = g_{m11}/C_L$)
- Zero cancelling resistor R_c moves z_1 towards the left half s plane and results in a third pole p_3
 - z_1 can be moved to ∞ with $R_c = 1/g_{m11}$
 - z_1 can be moved to cancel p_2 with $R_c > 1/g_{m11}$ (needs to be verified against process variations)
 - Third pole p_3 at a high frequency
- Poles and zeros from the first stage will appear in the frequency response— $Y_{m1}(s)$ instead of g_{m1} in V_o/V_i above
 - Mirror pole and zero
 - Poles due to cascode amplifiers

Compensation cap sizing

$$p_2 \approx -\frac{g_{m11} \frac{C_c}{C_1 + C_c}}{\frac{C_1 C_c}{C_1 + C_c} + C_L}$$

$$\omega_u \approx \frac{g_{m1}}{C_c}$$

Phase margin (Ignoring $p_3, z_1, \dots$)

$$\phi_M = \tan^{-1} \frac{|p_2|}{\omega_u}$$

$$\frac{|p_2|}{\omega_u} = \tan \phi_M$$

$$\frac{g_{m11}}{g_{m1}} \left(\frac{C_c}{C_L} \right)^2 = \frac{C_c}{C_L} \left(1 + \frac{C_1}{C_L} \right) \tan \phi_M + \frac{C_1}{C_L} \tan \phi_M$$

- For a given ϕ_M , solve the quadratic to obtain C_c/C_L
- If C_1 is very small, $p_2 \approx -g_{m2}/C_L$; further simplifies calculations

Two stage opamp

A_o	$g_{m1}g_{m11}/(g_{ds1} + g_{ds3})(g_{ds11} + g_{ds12})$
A_{cm}	$g_{ds0}g_{m11}/2g_{m3}(g_{ds11} + g_{ds12})$
C_i	$C_{gs1}/2$
ω_u	g_{m1}/C_c
p_k, z_k	See previous pages
S_{vi}	$\approx 16kT/3g_{m1}(1 + g_{m3}/g_{m1})$
σ_{Vos}^2	$\approx \sigma_{VT1}^2 + (g_{m3}/g_{m1})^2\sigma_{VT3}^2$
V_{cm}	$\geq V_{T1} + V_{DSAT1} + V_{DSAT0}$ $\leq V_{dd} - V_{DSAT3} - V_{T3} + V_{T1}$
V_{out}	$\geq V_{DSAT12}$ $\leq V_{dd} - V_{DSAT11}$
SR+	I_0/C_c
SR-	$\min\{I_0/C_c, I_1/(C_L + C_c)\}$
I_{supply}	$I_0 + I_1 + I_{ref}$